



Answer script submission  
mail ID  
scm.even.cmsg21@gmail.c  
om

**WEST BENGAL STATE UNIVERSITY**  
B.Sc. Honours/Programme 4th Semester Examination, 2022

**CM SHGEC04T/CM SGCOR04T-COMPUTER SCIENCE (GE4/DSC4)**

**COMPUTER SYSTEM ARCHITECTURE**

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.  
Candidates should answer in their own words and adhere to the word limit as practicable.*

**Answer Question No. 1 and any *four* questions from the rest**

1. Answer any *four* questions from the following: 2×4 = 8
  - (a) Define instruction set.
  - (b) Why CPU registers are preferred for temporary data storage?
  - (c) Define Fan-in of a gate.
  - (d) What is byte code?
  - (e) Draw an EX-OR gate using only NAND gate.
  - (f) Define min-term and max-term of a Boolean function.
  - (g) How to define a digital circuit?
  - (h) What is PCI?
2. (a) Define a decoder. Design a 3-to-8 decoder using 2-to-4 decoder. 4  
(b) Realize a full subtractor circuit using half subtractor. 4
3. (a) State and prove De Morgan's theorem by using truth table. 4  
(b) Simplify the following expression into SOP using K map 4  
$$F(a, b, c, d) = \sum m(0, 1, 2, 3, 7, 8, 10) + \text{don't care conditions } \sum d(5, 6, 11, 15).$$
4. (a) What is SR Flip-Flop? Draw NAND based SR Flip-Flop. 4  
(b) Derive the characteristic equation and excitation table of SR Flip-Flop. 4
5. (a) Convert  $(10101.010)_2$  to decimal number. 2  
(b) Perform the subtraction with 2's complement:  $(1111)_2 - (1010)_2$  3

- (c) Simplify the following expression using K-map: 3

$$F(P, Q, R) = P'Q'R' + P'QR' + PQ'R' + PQR' + PQR$$

6. (a) What do you mean by addressing mode? 2

- (b) Explain relative and indexed addressing modes with examples. 2+2

- (c) What is interrupt? 2

7. Write short notes on (any *two*): 4×2 = 8

- (a) Associative memory

- (b) Decoder-demultiplex circuit

- (c) Register addressing mode vs. Direct addressing mode

- (d) SRAM vs. DRAM.

**N.B. :** *Students have to complete submission of their Answer Scripts through E-mail / Whatsapp to their own respective colleges on the same day / date of examination within 1 hour after end of exam. University / College authorities will not be held responsible for wrong submission (at in proper address). Students are strongly advised not to submit multiple copies of the same answer script.*

—x—